

Welcome to

Electric Machines & Drives

thomasblairpe.com/EMD

Thomas Blair, P.E.
USF Polytechnic – Engineering
tom@thomasblairpe.com




Session 3:
DC Motors

Fall 2011




Session 3

➤ **Chapter 5 – DC Motors**



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

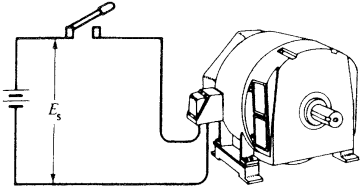

Chapter 5 – DC Motors



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5 – DC Motors

Constructed same as DC generator
Torque & Speed control with high efficiency
Starting methods






Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

$E_o = Z n \Phi / 60$

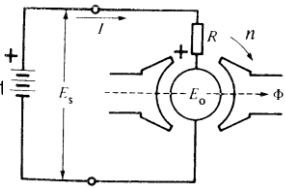E_o proportional to speed
At rest $E_o = 0$
At steady state
 $E_o = E_s - I \cdot R$
 $E_o =$ counter-electric force (CEMF)


Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

Starting Current many times running current
Speed ceases to increase when
Tload = Tmotor

$I = (E_s - E_o) / R$
 $I = E_s / R$ (during start)

6



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 5-1

The armature of a permanent magnet DC generator has a resistance of 1Ω and generates a voltage of 50V when the speed is 500 rpm. If the armature is connected to a source of 150V, calculate the following;

- The starting current
- The counter emf when the motor runs at 1000 rpm and at 1460 rpm
- The armature current at 1000 rpm and at 1460 rpm


7



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 5-1

Solution

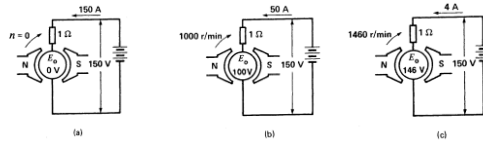

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

Mechanical Power & Torque

$$P = n T / 9.55 = E_o I$$

$$E_o = Z n \Phi / 60$$

- P = mechanical power developed by motor (W)
- E_o = induced voltage in armature (cemf) (V)
- I = total current supplied to the armature (A)

9



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 5-2

The following details are given on a 225kW (300HP), 250V, 1200rpm dc motor. Calculate

- The rated armature current
- The number of conductors per slot
- The flux per pole

armature coils	243
turn per coil	1
type of winding	lap
armature slots	81
commutator segments	243
field poles	6
diameter of armature	559 mm
axial length of armature	235 mm

10



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

Speed of Rotation – Proportional to E_s and inversely proportional to flux (field current)
Bonus Question, what happens to DC motor on Loss of Field Current?

$$N = 60 E_s / (Z \Phi) \text{ [approximately]}$$

- N = speed of rotation (rpm)
- E_s = armature voltage (V)
- Z = total number of armature conductors

11




Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

Speed control from MG set – controlling E_s

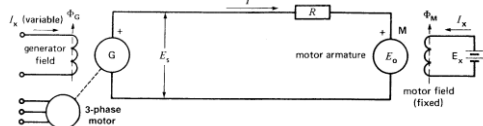- controlling I_x
- Can flow power in both directions due to MG set
- High efficiency



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 5-3

A 2000kW, 500V, variable speed motor is driven by a 2500KW generator, using a Ward Leonard control system. The total resistance of the motor and generator armature circuit is $10\text{ m}\Omega$. The motor turns at a nominal speed of 300 rpm, when E_o is 500V. Calculate

- The motor torque and speed when $E_s = 400\text{V}$ and $E_o = 380\text{V}$
- The motor torque and speed when $E_s = 350\text{V}$ and $E_o = 380\text{V}$

13




Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

Rheostat allows control of $E_o \rightarrow$ speed control

Efficiency very poor


Small motors only.

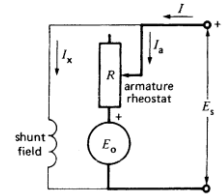

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

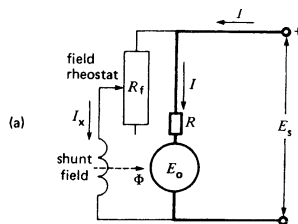
Speed control via field control
Flux increase \rightarrow speed decrease
Operate above base speed



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

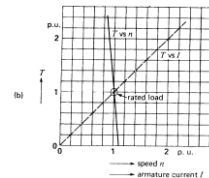As load increases, T_{load} increases, causing armature current to increase causing speed to drop
Speed regulation good (10%-20%)





Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

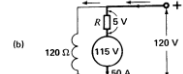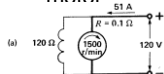Example 5-4

A shunt motor rotating at 1500 rpm is fed by a 120v source. The line current is 51A and the shunt field resistance is $120\ \Omega$. If the armature resistance is $0.1\ \Omega$, calculate the following;

- The current in the armature
- The counter emf
- The mechanical power developed by the motor



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)



Chapter 5

Series Motor – Different torque speed characteristic

Starting torque higher

Reduction in load = reduced flux = higher speed

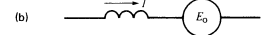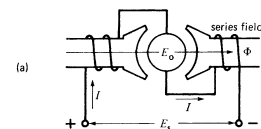
Bonus Question – what happens if load removed?



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

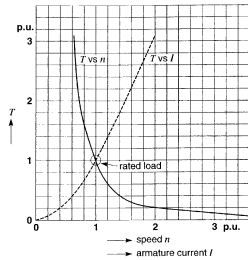As load decreases, Tload decreases, causing armature current to decrease causing flux to drop causing speed to increase rapidly Speed regulation poor




Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

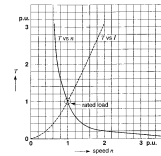Example 5-5

A 15hp, 240V, 1780 rpm dc series motor has a full load rated current of 54A. Its operating characteristics are given by the per unit curve of Fig 5.11. Calculate

- The current and speed when the load torque is 24 N m
- The efficiency under these conditions



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5


Compound DC Motor – Both series & shunt field
No load, shunt field controls max speed
Full load, series field adds to mmf -> increased flux -> speed decreases
Regulation 10% - 30%
Differential Compound – series field mmf subtracts from shunt field mmf

21



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)


Chapter 5

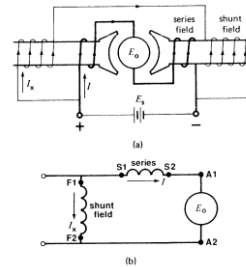

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

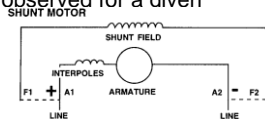
All connections CCW rotation facing OE of the drive. For clockwise rotation, interchange A1 and A2. Some manufacturers connect the interpole winding on the A2 side of the armature. When shunt field is separately excited, same polarities must be observed for a given rotation.



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

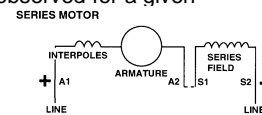
All connections CCW rotation facing OE of the drive. For clockwise rotation, interchange A1 and A2. Some manufacturers connect the interpole winding on the A2 side of the armature. When shunt field is separately excited, same polarities must be observed for a given rotation.



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

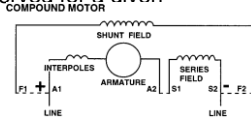
All connections CCW rotation facing OE of the drive. For clockwise rotation, interchange A1 and A2. Some manufacturers connect the interpole winding on the A2 side of the armature. When shunt field is separately excited, same polarities must be observed for a given rotation.



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5


Speed Torque

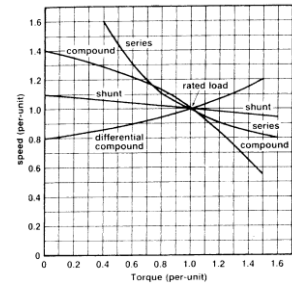

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

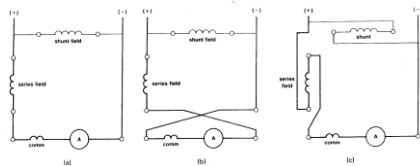
Direction of Rotation – Reverse Armature or Field
Commutation polarity associated with Armature polarity



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

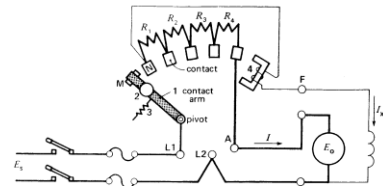
Current limitation during start –
Rheostat or resistor, solid state RVS



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

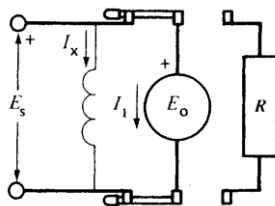Dynamic Breaking –
Speed proportional to E_o



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5


Motor becomes generator (direction of I reverses)
– E_o dissipates into R
-Torque reversed
-Brings machine to quicker stop




Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

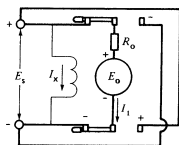Plugging – I is reversed on motor – resistor limit current
When motor stop, open circuit



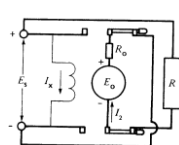
USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

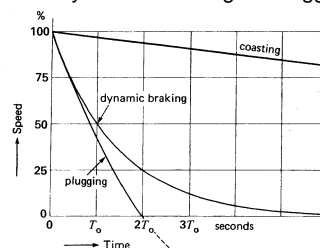Comparison of Dynamic Breaking vs Plugging



USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

Time Constant for Dynamic Breaking
T = time to reach 36.8% initial speed
T_O = time to reach 50% speed
Excludes windage and friction effects

$$T_o = 0.693 T = J n^2 / (131.5 P_1)$$

T = time for the motor speed to fall to ½ previous value (s)
J = moment of inertia referred to motor shaft (kg m²)
n₁ = initial speed (rpm)
P₁ = initial power on brake resistor (W)

33

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 5-6

A 225kW, 250V, 1280 rpm dc motor has windage, friction, and iron losses of 8kw. It drives a large flywheel and the total moment of inertia of the flywheel and armature is 177 kg m². The motor is connected to a 210V dc source, and its speed is 1280 rpm just before the armature is switched across a braking resistor of 0.2 Ω. Calculate

- The mechanical time constant T_o of the braking system
- The time for the motor speed to drop to 20 rpm
- Time for speed to drop to 20 rpm if the only braking force is that due to windage, friction, and iron losses

34

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

For Dynamic Brake t_s approx 5 * T_O

For Plugging -> t_s = 2 * T_O

t_s = stopping time using plugging (s)
T_o = time constant

35

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Example 5-7

The motor of example 5-6 is plugged and the braking resistor is increased to 0.4 Ω so that the initial braking current is the same as before. Calculate

- The initial braking current and braking power
- The stopping time

36

USF UNIVERSITY OF SOUTH FLORIDA POLYTECHNIC


Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

Armature reaction

-
- Neutral shift &
- Field weakening
- $\Phi_3 < \Phi_1$
- Commutating
- Poles


No load flux distribution

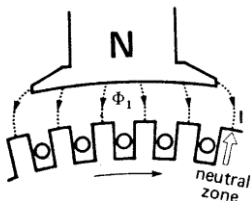


Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

Flux created by armature current

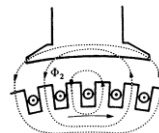

Resulting flux

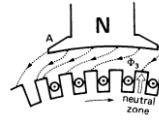

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

Variable Speed Control – (use PU values)

From base speed & torque –
To reduce speed, reduce E_a (T remains constant)

“Constant Torque” region.

To raise speed, reduce Φ_f (T decreases but P constant)

“constant HP” region. ($P \propto T * n$)

$T = \phi_f I_a$

$E_a = n \phi_f$


39



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5


Torque vs. Speed Curve

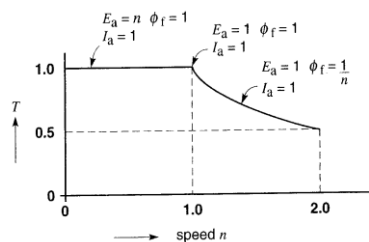

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

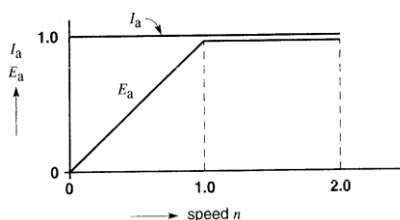
Armature voltage & current vs speed curves



Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5


Field flux vs speed curve

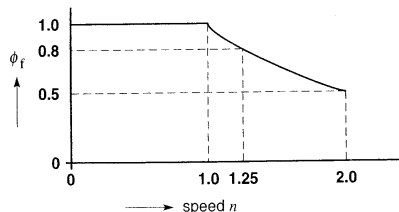

Electric Machines and Drives
Thomas Blair, P.E.
(tom@thomasblairpe.com)

Chapter 5

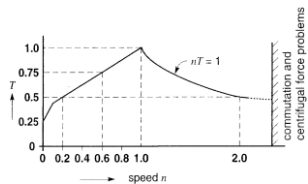Actual Torque vs Speed Curve –
 Low speed cooling limitations
 High speed commutation losses & centrifugal forces



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Chapter 5

PM Motors – no separate excitation, no loss of field concern
 Magnetic field does not distort like EM field.
 High cost & lack of field speed control



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

44

Chapters 6 and 13 next session



Electric Machines and Drives
 Thomas Blair, P.E.
 (tom@thomasblairpe.com)

Electric Machines & Drives

thomasblairpe.com/EMD



Thomas Blair, P.E.
 USF Polytechnic – Engineering
 tom@thomasblairpe.com



End of Session 3:
 DC Motors

Spring 2011